
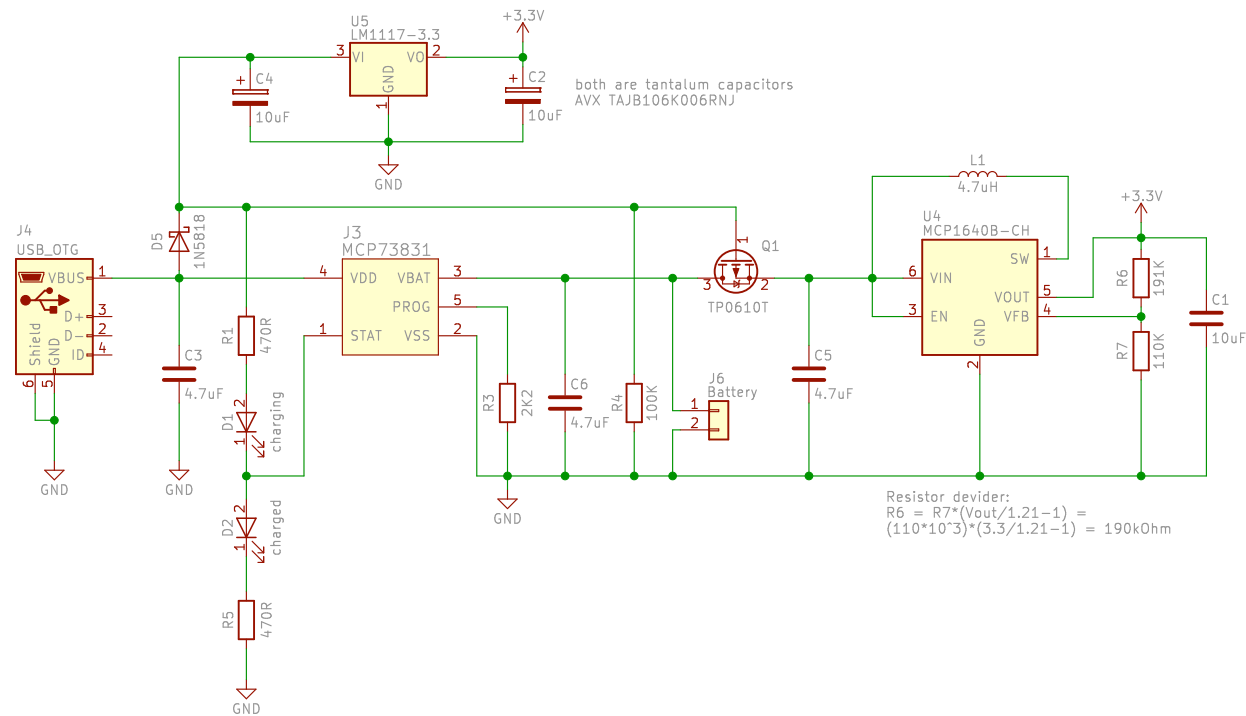




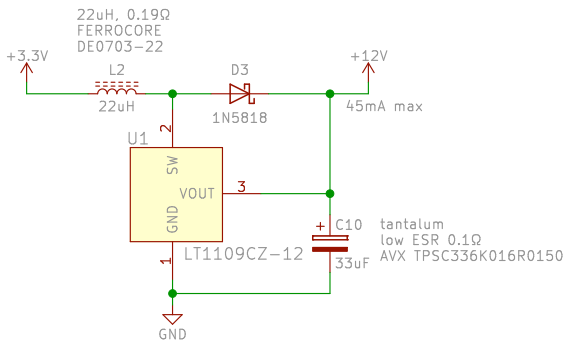
3.7V Li-Ion, Li-Polymer Battery Charger Circuit with Load Sharing



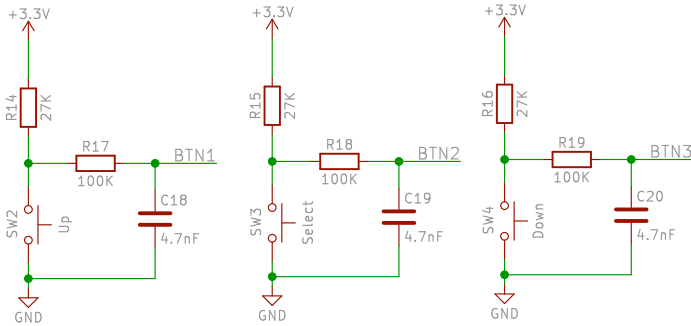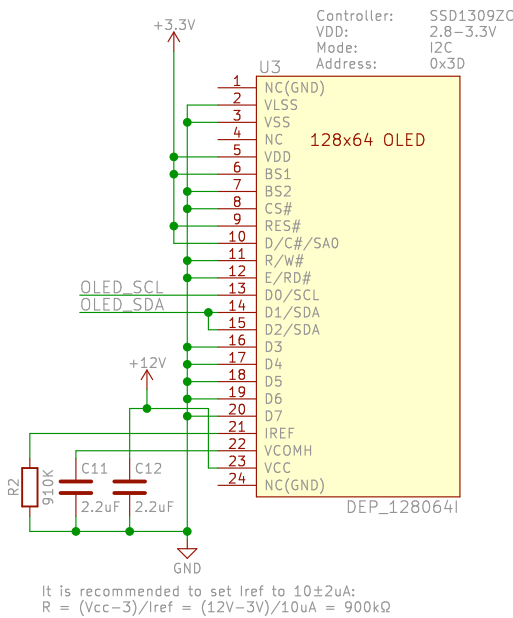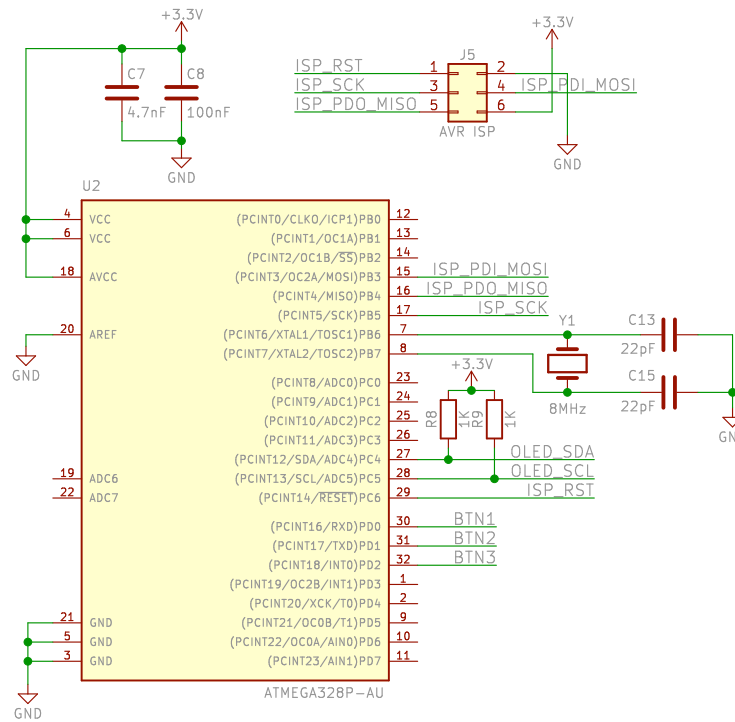3.3V to 12V, 45mA DC-DC for OLED panel



Power required from the inductor:
 $P_L = (V_{out} + V_d - V_{in}) \cdot I_{out} = (12V + 0.5V - 3.3V)(45mA) = 414mW$
Energy required by the inductor per cycle must be \geq :
 $P_L / f_{osc} = 414mW / 120kHz = 3.45 \mu J$
Picking an inductor value of $22\mu H$ with $0.19R$ DCR
results in a peak switch current of:
 $I_{peak} = (3.3V / (0.8R + 0.19R)) \cdot (1 - e^{-(1.0 \cdot 4.2us) / (22uH)}) = 579mA$
Once I_{peak} is known, energy in the inductor at the end
of the switch-ON time can be calculated as:
 $E_L = 0.5 \cdot (L \cdot I_{peak}^2) = 0.5 \cdot (22uH) \cdot (0.579)^2 = 3.69 \mu J > 3.45 \mu J$



1KIB